

PHYSQ 126 – Quiz 5 (3 mars 2016) **Solution**

Problem 21.86

The capacitor in an RC circuit is initially uncharged.

Part A

In terms of R and C , determine the time required for the charge on the capacitor to rise to 50% of its final value.

Express your answer in terms of the variables R and C .

$t =$

Submit

My Answers [Give Up](#)

Part B

In terms of R and C , determine the time required for the initial current to drop to 10% of its initial value.

Express your answer in terms of the variables R and C .

$t =$

Submit

My Answers [Give Up](#)

Solutions

86. **Picture the Problem:** A battery, a resistor, and a capacitor form a series RC circuit.

Strategy: Equation 21-18 determines the charge on a capacitor in a series RC circuit as a function of time. Solve equation 21-18 for the time required to charge the capacitor to 50% of its full charge. Then solve equation 21-19 for the time required for the current to drop to 10% of its initial value.

Solution: 1. (a) Set $q(t) = 0.50q_{\max} = 0.50C\mathcal{E}$
in equation 21-18 and solve for the time t :

$$0.50C\mathcal{E} = C\mathcal{E}(1 - e^{-t/RC})$$

$$0.50 = 1 - e^{-t/RC}$$

$$e^{-t/RC} = 1 - 0.50$$

$$-\frac{t}{RC} = \ln 0.50$$

$$t = -RC \ln 0.50 = \boxed{RC \ln 2.0}$$

2. (b) Set $I(t) = 0.10 I(0) = 0.10 \frac{\mathcal{E}}{R}$ and solve for t :

$$0.10 \frac{\mathcal{E}}{R} = \frac{\mathcal{E}}{R} e^{-t/RC}$$

$$0.10 = e^{-t/RC}$$

$$\ln 0.10 = -\frac{t}{RC} \Rightarrow t = \boxed{RC \ln 10}$$

Insight: When a single time constant has passed, the charge has increased from zero to 63.2% of its final value, and the current has dropped to 36.8% of its initial value.